

Name _____


Circuit Symbols

| | | | |
|---------|--|----------|--|
| Wire | | Resistor | |
| Lamp | | Switch | |
| Battery | | | |


Drawing Circuits

Before you build your different circuits draw a picture of your circuit using the proper symbols.

Series circuit

 

Parallel

 

What differences did you observe between the circuits in series and in parallel?